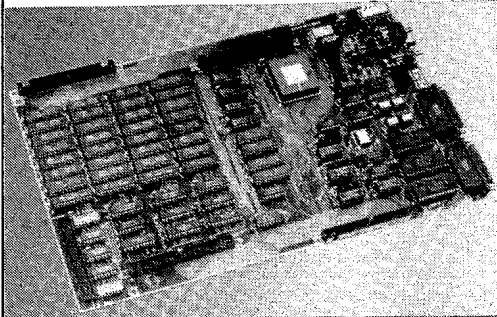


"FORTH GALORE"

NOVIX

8 mips forth engine




Available also for IBM-PC, STD Bus, VME Bus

READER INFO NO. 78

NB4000 Beta Board

- NC4016 16-bit high-speed microprocessor
- Fast 35 ns CMOS memory enables full processor speed (8MIPS)
- 28K words RAM for program/data storage and 4k words system ROM
- Hardware data stack and return stack each provide 256 16-bit cells per task
- Programmable selection of up to 8 stack segments allows multitask switching in less than 5 microseconds
- Dual serial RS232 I/O support
- A small computer standard interface
- Complete polyFORTH operating system/development environment

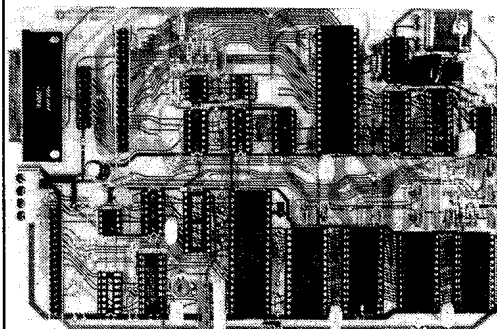

READER INFO NO. 79

EC-1F11 FORTH DEVELOPMENT SYSTEM

2MHz R65F11; Serial I/F; 5/4 Disc Drive Controller; 6K RAM; Expandable Shortform kit available. Excellent for Development

Also available

EC-111 SBC with 24I/O; 8 x A/D; 2 x D/A; Serial I/F; 24K Memory; watchdog; 2 MHz & Forth EC-1F12. Minimum System R65F12AQ. 16K Memory I/O, Serial I/F, Forth. Kernel. Economic EC-1F11 AD 10 bit AD, R65F12AQ watchdog upgrade for EC-1F11

energy CONTROL

Energy Control Pty Ltd

P.O. Box 6502, Goodna, Qld 4300 26 Boron St, Sumner Pk, Qld 4074
Phone: (07) 376 2955 Telex: AA43778 ENECON Fax: (07) 376 3286

READER INFO No. 30

80 — ETI August 1987

ETI-184 IC

Circuit Digital Tester

In-Circuit Digital IC Tester

Yet another cheap, easy and useful test device from ETI.

THIS VERY SIMPLE project allows digital integrated circuits to be tested, whilst in circuit.

Using an ic test clip clamped over the device to be tested, a series of Light Emitting Diodes indicate whether the pins on the ic are going high, low, or switching. Working with a manual or data sheet for the particular ic, this LED indication will show how the ic is functioning.

The standard project uses a 16 pin test clip, allowing up to 18 pin devices to be checked. This can be done by applying the clip in two stages, so as to cover all the pins. The same method will allow you to check 40 pin devices using a 24 pin clip. Due to changes in ic width versus pin numbers, different size clips are necessary.

The project can be used on digital ic's from 5 Vdc to 22 Vdc (on the pins). The current rate is set at 3 mA for 5 Vdc, and 20 mA for 22 Vdc. Note: Inputs and outputs below 3 mA may not have sufficient current to light the LED — but if there is less than 3 mA going to the ic then it probably wouldn't trigger anyway.

Voltages below 1.8 Vdc are considered "lows", and greater than 2 Vdc are considered "highs". The trigger voltages for the LED's are provided by the ic pins switching high or low.

By using a data reference for the ic being checked (this can come from the circuit or a data manual) it is possible to establish if the ic is functioning correctly.

HOW TO USE

Clip the test clip onto the ic — making sure that pin 1 of the ic matches pin 1 of the clip.

Any lit LED means that on that pin there is a high, unlit LED's infer a low, and flickering LED's indicate that the pin is switching high/low.


It's with the same body width as the test


clip being used, but with a greater number of pins, require two stage checking. Follow the above procedure, and after testing the first 16 or 24 pins, remove the clip and re-clamp it onto the remaining pins.

CONSTRUCTION

Construction is very simple, and has been made easier through the use of a Printed Circuit Board. Start by soldering R1 (1k2 1 Watt) onto the pc board. Next, place the LED's on the board but do not solder yet. Push the LED's into the panel (pre-punched) ensuring that they have a firm, tight fit, and are all level. Wriggle the pc board down the LED leads as far as possible to the bases of the LED's. Now solder the LED's.

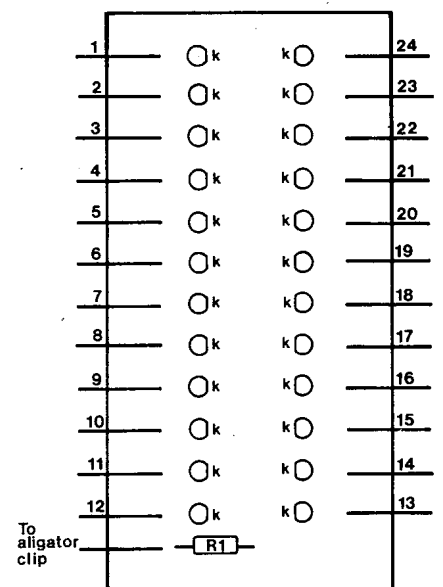Cut a slot, or drill a hole in the side of the case to accept the rainbow cable. Then drill a small hole for the common flying



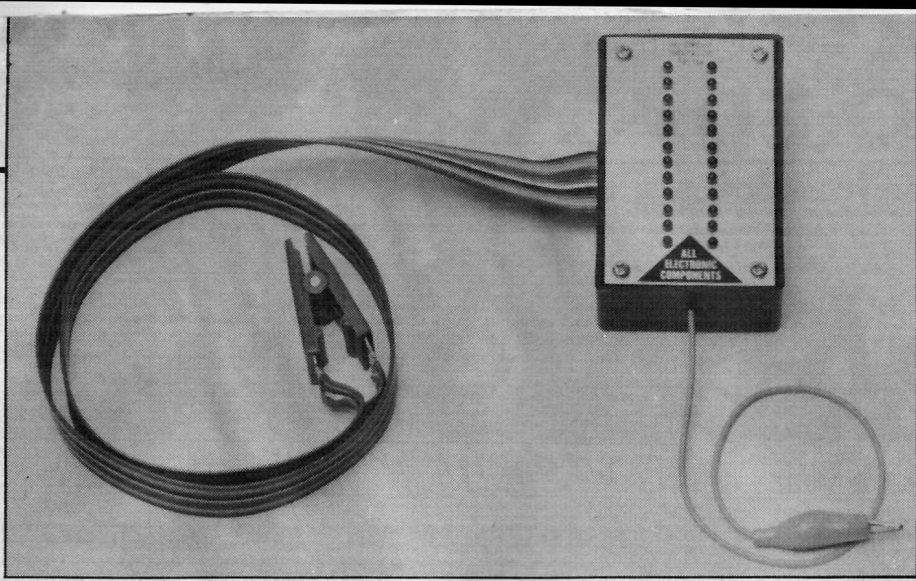

lead. On the lead, solder the alligator clip on one end, and the other end to the board.

Solder the rainbow cable to the test clip — we found it best to solder the first wire to pin 1 of the clip, and the second wire to the pin opposite pin 1, and so on. This avoids bending and twisting the cable. With a black marker pen or texta, mark pin 1 of the test clip for identification.

All that remains is to solder pin 1 of the test clip to the pc board on LED 1, and so on.


To check that the unit is functioning correctly, use a supply between 5 Vdc and 20 Vdc — a 9V battery will do. Clip the

alligator clip to the negative terminal of the supply and check that the correct LED lights with the correct pin on the test clip, from the positive of the supply.

**PARTS LIST
ETI-184**

- R1 1k2 1 watt 5% Resistor
- LED1-24 3mm Red LED
- PCB AEC 87-5-1 Single-sided tinned.
- PANEL Silk-screened aluminium.
- TC1 16 pin ic Test Clip.
- CASE UB5
- MISCELLANEOUS 1 metre 24 way Rainbow cable, 1 metre hook-up wire, Alligator clip, solder.

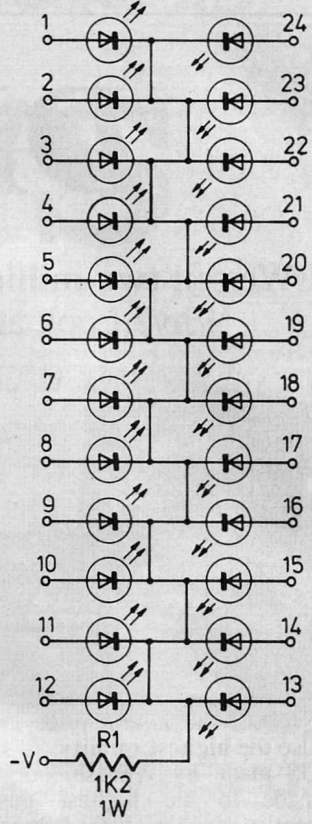
This project was designed by the technical staff at All Electronic Components.



All Electronic Components.

118 – 122 LONSDALE STREET MELBOURNE, VIC. 3000. AUSTRALIA.

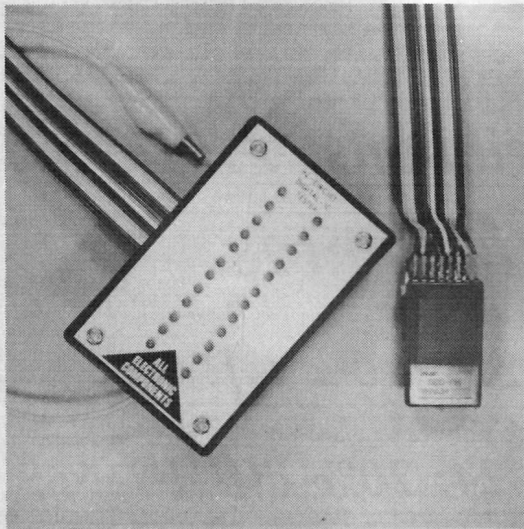Telephone : (03) 662 3506 Fax : (03) 663 3822.



\$39.95

MAIL ORDER SPECIAL OFFER .

To launch the first of our NEW range of ALL ELECTRONIC COMPONENTS kitsets , we have decided to eliminate freight charges on this item for THIS MONTH ONLY. Just clip out the coupon below — a photocopy, or a letter with the same details will suffice — and send it to us before the end END OF THIS MONTH with your remittance.

And don't forget — we stock a huge range (easily the largest in Australia) of ETI – EA – AEM – HE & AEC. kitsets. Just ask for your FREE catalogue.



PLEASE SEND ME THE FOLLOWING :

QTY IN CIRCUIT DIGITAL I.C. TESTER KITSETS @ \$39.95 EACH.

Sub Total — \$:

NAME :
 ADDRESS :
 STATE :P/CODE :

Freight — FREE.

TOTAL — \$:

Card No :
 Expiry Date : Signature :

CHEQUE MONEY ORDER BANK CARD AMEX